

Sintek ewation

and the local division of the local division

www.gew.co.za

Gert Veale / Christo Nel Grintek Ewation



- Where are RF synthesizers used ?
- What is phase noise ?
- Phase noise effects
- Classic RF synthesizer architecture
- VCO phase noise modification
- In-band phase noise floor
- Optimum PLL loop bandwidth
- Conclusions





- Local oscillators (LOs) in receiver or transmitter architectures
- Digital clocks for analogue to digital converters (ADCs), digital to analogue converters (DACs) and other digital circuitry.



• In the time domain it can be seen as jitter on a signal:



• In the frequency domain it presents itself as noise sidebands:



Page 4



Mathematical Definition:





• Receiver reciprocal mixing with a noisy LO:



• Effect: Reduced receiver sensitivity in the presence of strong signals



• ADC clock with jitter:



$$SNR_{FS} = -20\log(2\pi f_{analogue} \Delta t_{RMS})$$
 (dB)

ADC Clock with jitter

- Result: Reduced full scale dynamic range
- Digital communication systems:
 - Result: Increased bit error rates (BERs) in phase modulated systems (QPSK, QAM etc.)



• Consist of a classic phase locked loop (PLL) architecture:



- Phase frequency detector (PFD)
- Loop filter
- Voltage controlled oscillator (VCO)
- Divider (N)



• VCO free running phase noise profile is altered by a PLL:



- An in-band noise floor $\mathcal{L}_{ ext{in-band}}$ is formed within the PLL loop bandwidth $\omega_{
 ho}$
- You can "clean up" a noisy VCO with a well designed PLL



 Consider the PLL linear model where each component has an associated noise source:





• More exact:

$$\mathcal{L}_{in-band}(\Delta f) \propto 20 \log N$$

$$\mathcal{L}_{in-band}(\Delta f) = 20 \log N + \mathcal{L}_{PFD}(\Delta f)$$

$$= 20 \log N + 10 \log f_{ref} + FOM$$



- Interesting: $\mathcal{L}_{PFD}(\Delta f)$ increases with PFD operating frequency f_{ref}
- Figure of merit (FOM) or normalized noise floor (\mathcal{L}_{1Hz}) is device specific
- FOM is mainly determined by the random noise or time jitter inside the PFD:

$$FOM = \mathcal{L}_{1Hz} = 20\log(2\pi\Delta t_{PFD})$$

 The specific IC semiconductor process (CMOS, SiGe, GaAs etc.) has a huge impact on the FOM



Commercial RF synthesizer IC FOM comparison:

Device	Max Freq.	<i>N</i> -Divider	IC Process	FOM $\mathcal{L}_{_{1Hz}}$	Power	Manufacturer
ADF4108	8 GHz	992 - 262175	0.35 µm BiCMOS	-119 dBc/Hz	0.08 W	Analog Devices
HMC700	8 GHz	32 - 65567	0.35 µm SiGe HBT	-226 dBc/Hz	0.36 W	Hittite Microwave
HMC440	2.8 GHz	2 - 32	GaAs HBT	-233 dBc/Hz	1.25 W	Hittite Microwave
HMC698	7 GHz	12 - 259	GaAs HBT	-233 dBc/Hz	1.55 W	Hittite Microwave

- Heterojunction bipolar transistor (HBT) designs tend to have better FOMs (Why ?)
- Devices with low N-Divider values and good FOMs normally dissipate a lot of power (Why ?)



• FOM dependant on PFD noise, In a typical tri-state CP PFD we have:



- t_{delay} is inserted to avoid the dead zone in the PFD
- Dead zone occurs when the current switches are not fast enough

 (A^2)

- Charge pump noise current: $\overline{i_{CP}^2} \propto \frac{t_{delay}}{T_{ref}} \cdot I_{CP} \Delta f$
- If designing a PFD, reduce t_{delay} for less PFD jitter and hence a better FOM:

 $FOM = 20\log(2\pi\Delta t_{PFD})$



- Calculate $\mathcal{L}_{in-band}$ from device FOM and average N-divider etc.
- Compare with VCO datasheet and set PLL loop bandwidth ω_p to the VCO phase noise offset frequency that intersects with $\mathcal{L}_{\text{in-band}}$



- An incorrect loop bandwidth will cost you unnecessary phase noise
- Too small a loop bandwidth will also increase the PLL lock time



- Phase noise in synthesizers and its effects were shown
- The concept of PLL in-band phase noise was demonstrated
- To minimize PLL in-band phase noise, the following can be done:
 - Use low N-divider values
 - Use a high reference or PFD frequency f_{ref} (This will reduce the N-divider)
 - Use a device with a good FOM
- Optimize the PLL loop bandwidth for a given VCO phase noise profile